

# Digital Logic Laboratory

Lab #1 – Report

Ana Maghradze

16th October 2021

## Contents

<b>1</b>	<b>Description of The Assignment</b>	<b>3</b>
<b>2</b>	<b>Description of The Solution</b>	<b>3</b>
<b>3</b>	<b>ModelSim Simulation</b>	<b>4</b>
<b>4</b>	<b>Appendix</b>	<b>5</b>

## 1 Description of The Assignment

In this assignment, we implement press multiplier on FPGA. We should have 4 different stages, use Key[0] to go from one stage to another and Key[1] to change the values of press\_counter\_A and press\_counter\_B – the numbers that we need to multiply.

When Key[0] is pressed, program goes to the first stage and LED[0] is ON. We should be able to increment press\_counter\_A by pressing key[1] at first stage. If Key[0] is pressed again, program goes to the second stage, LED[0] and LED[1] are ON and we should be able to increment press\_counter\_B by pressing key[1]. If Key[0] is pressed again, program goes to the third stage and the result of the multiplication of press\_counter\_A and press\_counter\_B should appear on LEDs. If Key[0] is pressed again, the program returns to the initial stage.

## 2 Description of The Solution

In the code, together with the inputs - CLOCK\_50 and KEY, I had to use 4 registers: stage, press\_counter\_A, press\_counter\_B, and prevKey.

2-bit register – prevKey holds the previous value of the KEY. I need this register to detect the change from previous value to the new value of KEY and, by this way, avoid the incorrect output caused by pressing on the button as its value remains the same for greater time than we need it to be. So, at the end of the always block, I write the KEY value into the prevKey.

On the positive edge of the clock, I check the values of KEY[0] and prevKey[0] together and KEY[1] and prevKey[1] together.

If KEY[0] is pressed, stage is changed. From the 3rd state everything goes to the 0th stage again.

We need KEY[1] only in 2nd and 3rd stages – if it's pressed, on the first stage press\_counter\_A is incremented, on the second stage press\_counter\_B is incremented.

If stage changed from 3 to 0, press\_counter\_A and press\_counter\_B values become 0s.

LED value on 0th, 1st or 2nd stage is the value of the stage itself, on the 3rd stage its value becomes the multiplication result.


### 3 ModelSim Simulation

```

11 initial begin
12     // key[0] is ON, go to stage 1
13     #10 key = 2'b01;
14     // in stage 1 increment press_counter_A when key[1] is pressed
15     #10 key = 2'b10; // press_counter_A = 1
16     #10 key = 2'b00;
17
18     #10 key = 2'b10; // press_counter_A = 2
19     #10 key = 2'b00;
20
21     #10 key = 2'b10; // press_counter_A = 3
22     #10 key = 2'b00;
23
24     // go to stage 2,
25     #10 key = 2'b01;
26     // in stage 2 increment press_counter_B when key[1] is pressed
27     #10 key = 2'b10; // press_counter_B = 1
28     #10 key = 2'b00;
29
30     #10 key = 2'b10; // press_counter_B = 2
31     #10 key = 2'b00;
32
33     // go to stage 3
34     #10 key = 2'b01;
35     #10 key = 2'b00;
36
37     // go to stage 0
38     #10 key = 2'b01;
39     #10 key = 2'b00;
40 end

```

Figure 1: testbench

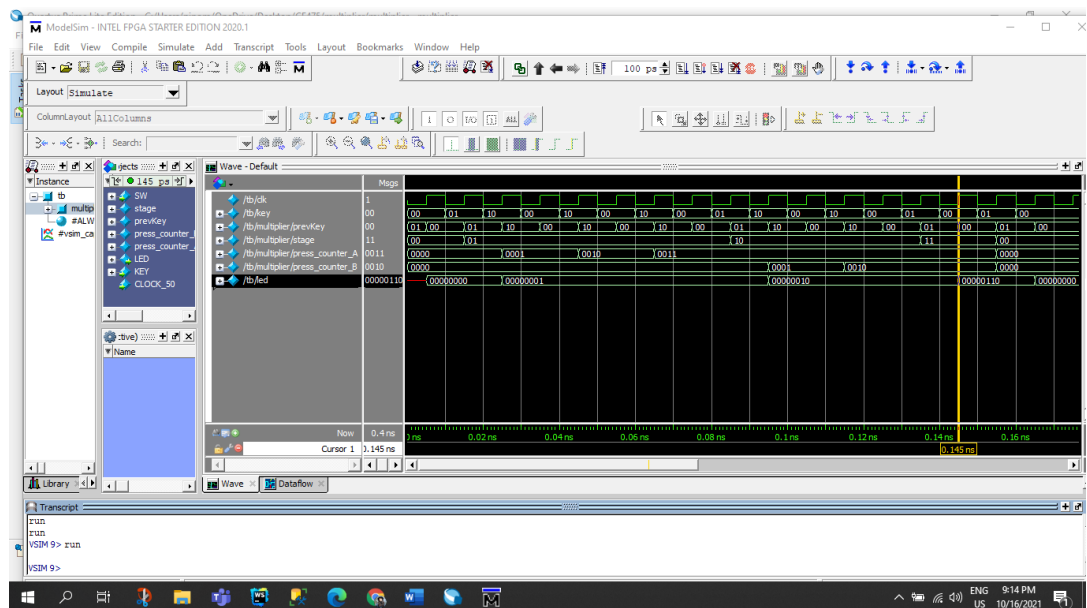

## 4 Appendix

```
module de0_nano_soc_baseline(  
    input  CLOCK_50,  
    input  [1:0] KEY,  
    input  [3:0] SW,  
    output reg [7:0] LED  
);  
    reg [1:0] stage = 0;  
    reg [1:0] prevKey = 1;  
    reg [3:0] press_counter_A = 0;  
    reg [3:0] press_counter_B = 0;  
  
    always @(posedge CLOCK_50)  
    begin  
        if(KEY[0] == 1 && prevKey[0] == 0)  
        begin  
            press_counter_A <= stage == 3 ? 0 : press_counter_A;  
            press_counter_B <= stage == 3 ? 0 : press_counter_B;  
  
            stage <= stage == 3 ? 0 : stage + 1;  
        end  
  
        if(KEY[1] == 1 && prevKey[1] == 0)  
        begin  
            press_counter_A <= stage == 1 ? press_counter_A + 1 : press_counter_A;  
            press_counter_B <= stage == 2 ? press_counter_B + 1 : press_counter_B;  
        end  
  
        LED[7:0] <= stage == 3 ? press_counter_A * press_counter_B : stage;  
        prevKey[1:0] <= KEY[1:0];  
  
    end  
endmodule
```

### TESTBENCH

```
module tb;  
    reg clk = 0;  
    reg [1:0] key = 0;  
    reg [3:0] sw = 0;  
    wire [7:0] led;  
  
    de0_nano_soc_baseline multiplier(clk, key, sw, led);  
  
    always #5 clk <= ~clk;  
  
    initial begin  
        // key[0] is ON, go to stage 1  
        #10 key = 2'b01;  
        // in stage 1 increment press_counter_A when key[1] is pressed  
        #10 key = 2'b10; // press_counter_A = 1  
        #10 key = 2'b00;  
  
        #10 key = 2'b10; // press_counter_A = 2  
        #10 key = 2'b00;  
  
        #10 key = 2'b10; // press_counter_A = 3  
        #10 key = 2'b00;  
  
        // go to stage 2,
```

```
#10 key = 2'b01;
// in stage 2 increment press_counter_B when key[1] is pressed
#10 key = 2'b10; // press_counter_B = 1
#10 key = 2'b00;

#10 key = 2'b10; // press_counter_B = 2
#10 key = 2'b00;

// go to stage 3
#10 key = 2'b01;
#10 key = 2'b00;

// go to stage 0
#10 key = 2'b01;
#10 key = 2'b00;
end

endmodule
```